

Solutions for Your Success™

Part #, Keyword, Crossference

Home > FLS2100XS

FLS2100XS Datasheet



Sample

Print

Email

More...

Back to Top

Favorite

FLS2100XS for 400W- Half-Bridge LLC Resonant Control IC for Lighting

Table of Contents:

General Description

Product Status/Pricing/Packaging

Support

Engineering Connections

Qualification Support Features Applications/Block Diagram(s)

Application Notes

General Description

The FLS-XS series of general lighting power controllers includes highly integrated power switches for medium - to high-power lumens applications. Offering everything necessary to build a reliable and robust half -bridge resonant converter, the FLS-XS series simplifies designs and improves productivity, while improving performance. The FLS-XS series combines power MOSFETs with fastrecovery type body diodes, a high-side gate-drive circuit, an accurate current controlled oscillator, frequency limit circuit, soft-start, and built-in protection functions. The high-side gate-drive circuit has common -mode noise cancellation capability, which guarantees stable operation with excellent noise immunity. The fastrecovery body diode of the MOSFETs improves reliability against abnormal operation conditions, while minimizing the effect of reverse recovery. Using zero voltage switching (ZVS) dramatically reduces the switching losses and significantly improves efficiency. ZVS also reduces switching noise noticeably, which allows a smallsized Electromagnetic Interference (EMI) filter.

The FLS-XS series can be applied to resonant converter topologies such as series resonant, parallel resonant, and LLC resonant converters.

Product Status/Pricing/Packaging

Back to Top

- Fairchild 1,000 piece Budgetary Pricing. *
- If there is no sample button displayed at the top of the page, please contact one of the Fairchild distributors or your local sales office to obtain samples.
- Top mark packaging information for product FLS2100XS is available. **

Product	Product Status	Eco Status	*Pricing	Package Type	Leads	Packing Method	Package Drawing	**Package Marking Convention	RoHS IPC1752	RoHS/REACH/JIG Certificate of Compliance
FLS2100XS	Full Production	Green by design	\$2.67	<u>SIP</u>	9	RAIL		Line 1: \$Y (Fairchild logo) & Z (Asm. Plant Code) &E& 3 (3-Digit Date Code) &K Line 2: FLS2100XS	XML	

Back to Top Support

- Knowledgebase (online Q&A)
- Find a local sales office
- Product change notices (PCN)
- How to Buy Products or Order Samples

Features

Back to Top

- Variable Frequency Control with 50% Duty Cycle for Half-Bridge Resonant Converter Topology
- High Efficiency through Zero Voltage Switching (ZVS)
- Internal UniFET™ with Fast -Recovery Body Diode
- Fixed Dead Time (350ns) Optimized for MOSFETs
- Up to 300kHz Operating Frequency
- Auto-Restart Operation for All Protections with External LV_{CC}
- Protection Functions: Over-Voltage Protection (OVP), Over-Current Protection (OCP), Abnormal Over-Current Protection (AOCP), Internal Thermal Shutdown (TSD)

Engineering Connections

Back to Top





Watch our Videos on YouTube



Check out our Podcasts on iTunes



Qualification Support

Back to Top

Customer qualification data for the FLS2100XS

Applications/Block Diagram(s)

Back to Top

- General LED Lighting
- Industrial, Commercial, and Residential LED **Lighting Fixtures**
- Outdoor Lighting: Street, Roadway, Parking, Construction and Ornamental LED Lighting

Application Notes

Back to Top

- AN-9729: LED Application Design Guide Using Half -Bridge LLC Resonant Converter for 100W Street Lighting (814 K) Oct 14, 2011
- AN-9730: LED Application Design Guide Using Half -Bridge LLC Resonant Converter for 160W Street Lighting (820 K) Oct 14, 2011

Browse All Application Notes

Products | Applications | Design Support | About Fairchild

Investor Relations | Careers | Contact Us | Site Map |

Privacy Policy | Site Terms & Conditions | Standard Terms & Conditions of Sale

© Copyright 2011 Fairchild Semiconductor. All rights reserved.

